


## “Gateway” lab exercises

1. [HelloWorld](#) - Making a new project with a *module* and controlling a single LED with a button.
2. [Hello lots of Worlds](#) - making a *bus* to wire all switches to all LEDs; the UCF (User Constraints File).
3. [HelloWorldSynchronous](#) - using *registers* and *wires*, simulation with a verilog *test fixture*; the *sensitivity list* in always@ in simulation. “If within a module you have a signal that is on the left hand side of an assignment within an ‘always@(..)’ statement, then it needs to be defined as a register (‘reg’).”
4. [ShiftingTheWorld](#) - synthesizing a shift register with *fd D-FlipFlops* using gate level and behavioral level design; *register transfer level (RTL)* design; *module instantiation*; *signalconcatenation*; introduction to *generate*.
5. [ShiftingManyWorlds](#) - 2d array of shift registers (memory); simulation exercise.
6. [CountingWorlds](#) - simple arithmetic, *multiplexing*.

## “Gateway” lab exercises

4. [ShiftingTheWorld](#) - synthesizing a shift register with *fd D-FlipFlops* using gate level and behavioral level design; *register transfer level (RTL)* design; *module instantiation*; *signalconcatenation*; introduction to *generate*.
5. [ShiftingManyWorlds](#) - 2d array of shift registers (memory); simulation exercise.
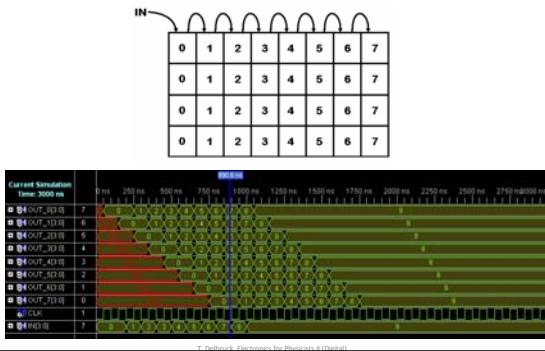
## 5. Shifting many worlds (simulation-only exercise)



## “Gateway” lab exercises

6. [CountingWorlds](#) - simple arithmetic, *multiplexing*.
7. [TimingTheWorld](#) - a second-counter watch using two counters, one clocking the other, both up/down with enable.
8. [DecodingTheWorld](#) - Number representation; 7-segment display *decoder* (see [BASYS2 manual](#)). See [7seg](#) for the code for this exercise.
9. [TimingTheWorldInDecimal](#) - multiple counters, using *generics* to instantiate modules with parameters; revisit *generate*.

## 6. Counting the world

Arithmetic, multiplexing, +/-, if/else


**On the rising edge** of the signal from the Button, if the control signal from the slide switch is '1' then the number stored in the register takes the value of the number stored in the register **plus** one. Else then the number stored in the register takes the value of the number stored in the register **minus** one.

```


21 module CountingWorlds(
22   input BUTTON,
23   input CONTROL_SWITCH,
24   output [7:0] LEDS
25 );
26
27   reg [7:0] Value;
28
29   always@ (posedge BUTTON) begin
30     if (CONTROL_SWITCH)
31       Value <= Value + 1;
32     else
33       Value <= Value - 1;
34
35   assign LEDS = Value;
36
37 endmodule
38
39

```

## RTL schematic

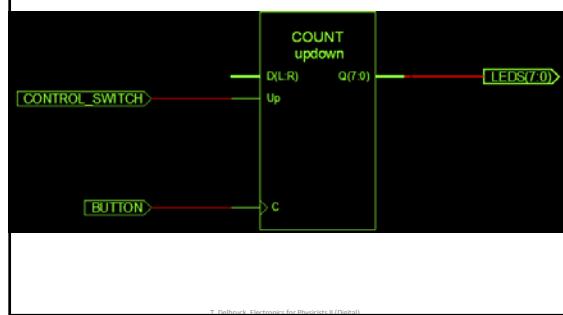
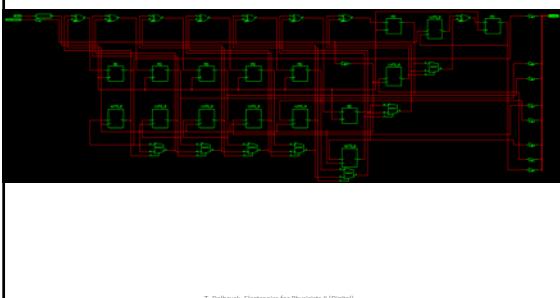
## Technology schematic for counting up/down




## "Gateway" lab exercises

6. [CountingWorlds](#) - simple arithmetic, **multiplexing**.
7. [TimingTheWorld](#) - a second-counter watch using two counters, one clocking the other, both up/down with enable.
8. [DecodingTheWorld](#) - Number representation; 7-segment display *decoder* ([see BASYS2 manual](#)). See [7seg](#) for the code for this exercise.
9. [TimingTheWorldInDecimal](#) - multiple counters, using **generics** to instantiate modules with parameters; revisit *generate*.
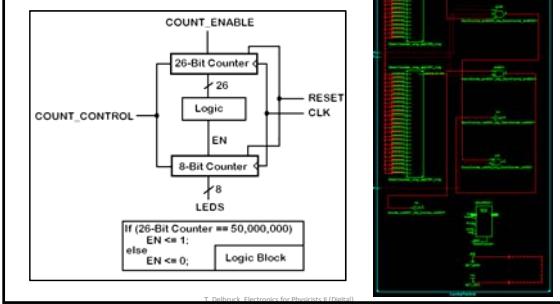
## 7. Timing the world

- Using on-board clock (instead of switch)
- Multiplexing



```
`timescale 1ns / 1ps
module counter(
    input CLK,
    input UP,
    input RESET,
    input ENABLE,
    output [7:0] LEDS
);
reg [7:0]value;
reg [24:0] downCounter;
always@(posedge CLK) begin
    if(RESET)
        downCounter<=0;
    else begin
        if(ENABLE) begin
            if(UP)
                if(downCounter==25000000)
                    downCounter<=0;
            else
                downCounter<=downCounter+1;
        end
        else begin
            if(downCounter==0)
                downCounter<=25000000;
            else
                downCounter<=downCounter-
1;
        end
    end
end
endbegin
T_Delbruck_Electronics_if(downCounter==0)
```

```
always@(posedge CLK) begin
    if(RESET)
        downCounter<=0;
    else begin
        if(ENABLE) begin
            if(UP)
                if(downCounter==25000000)
                    downCounter<=0;
                else
                    downCounter<=downCounter+1;
            end
            else begin
                if(downCounter==0)
                    downCounter<=25000000;
                else
                    downCounter<=downCounter-
1;
            end
        end
    end
end
endbegin
T_Delbruck_Electronics_if(CLK)
```

```
always@(posedge CLK) begin
    if(RESET)
        value<=0;
    else begin
        if(downCounter == 0) begin
            if(UP)
                value <= value + 1;
            else
                value <= value - 1;
        end
    end
end
assign LEDS=value;
endmodule
T_Delbruck_Electronics_if(CLK)
```

```

NET "UP" LOC="P11"; // SW0 controls up / down
NET "ENABLE" LOC=L3; // SW1 must be up to count
NET "RESET" LOC=C11; // BTN1 resets counter
NET "CLK" LOC=B8; // global clock @ default
50MHz
NET "LEDS<7>" LOC="G1";
NET "LEDS<6>" LOC="P4";
NET "LEDS<5>" LOC="N4";
NET "LEDS<4>" LOC="N5";
NET "LEDS<3>" LOC="P6";
NET "LEDS<2>" LOC="P7";
NET "LEDS<1>" LOC="M11";
NET "LEDS<0>" LOC="M5";

```

T. Dohrbeck, Electronics for Physicists II (Digital)


## "Gateway" lab exercises

6. [CountingWorlds](#) - simple arithmetic, **multiplexing**.
7. [TimingTheWorld](#) - a second-counter watch using two counters, one clocking the other, both up/down with enable.
8. [DecodingTheWorld](#) - Number representation; 7-segment display **decoder** (see [BASYS2 manual](#)). See [7seg](#) for the code for this exercise.
9. [TimingTheWorldInDecimal](#) - multiple counters, using **generics** to instantiate modules with parameters; revisit **generate**.


T. Dohrbeck, Electronics for Physicists II (Digital)
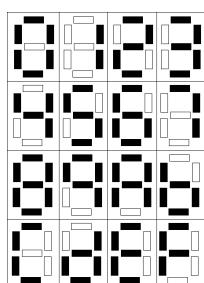
## 8. Decoding the world


- Combinational logic, Karnaugh maps
- Module reuse with wrappers



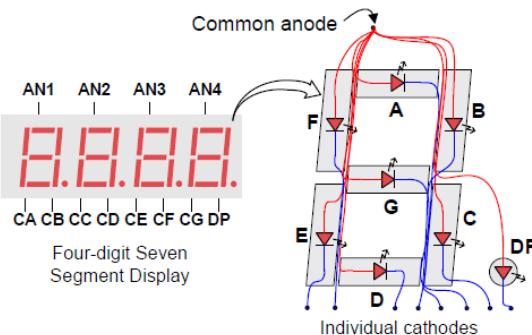T. Dohrbeck, Electronics for Physicists II (Digital)









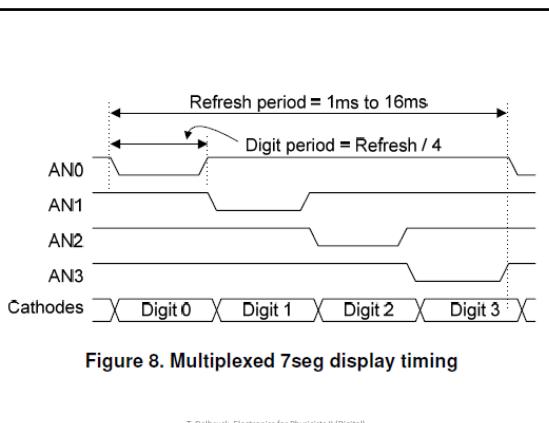
T. Dohrbeck, Electronics for Physicists II (Digital)



T. Dohrbeck, Electronics for Physicists II (Digital)


## Karnaugh map for segment CA

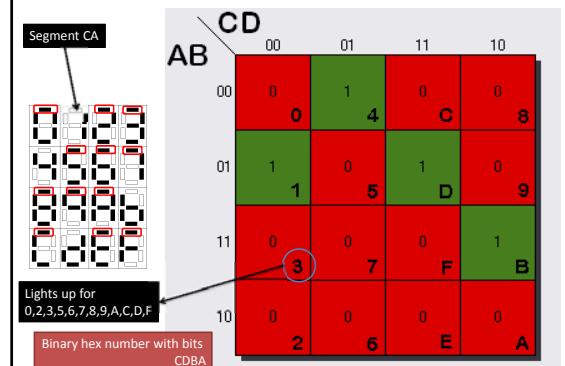

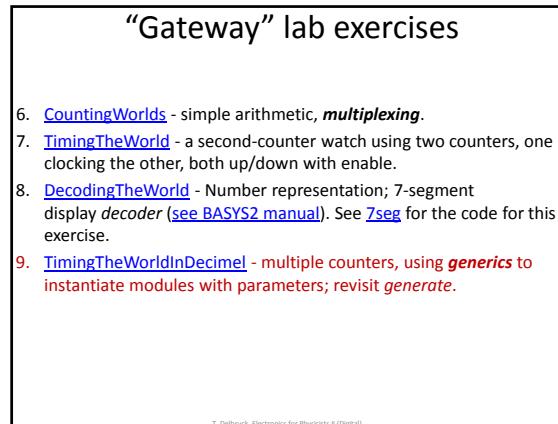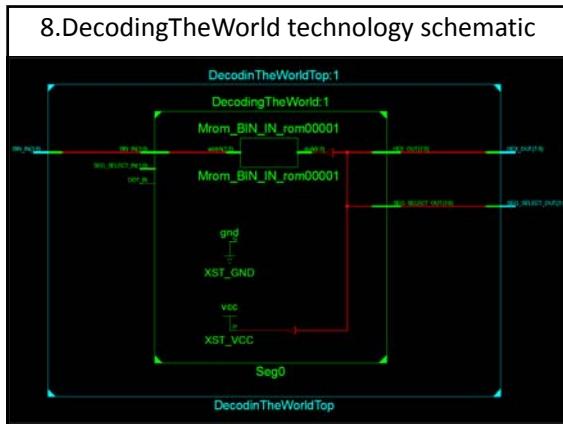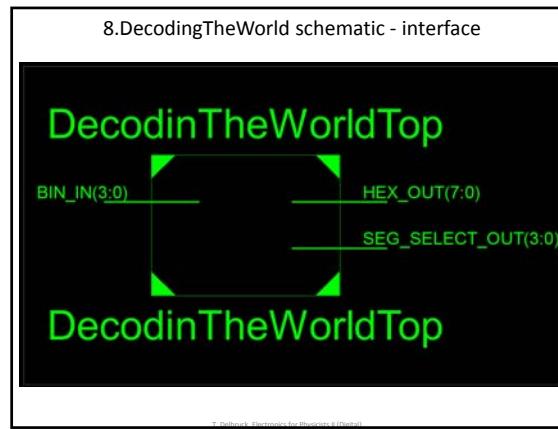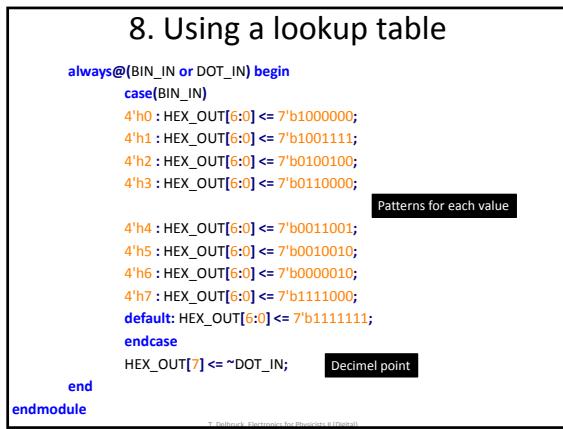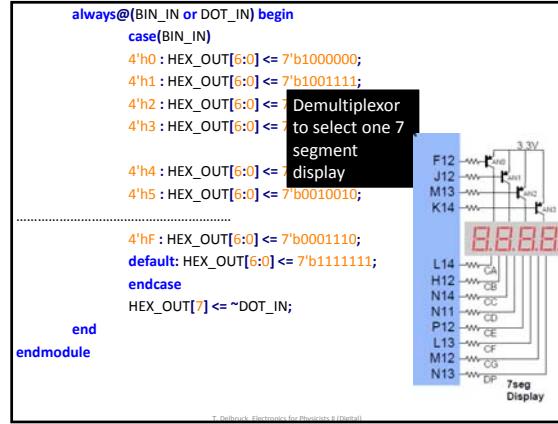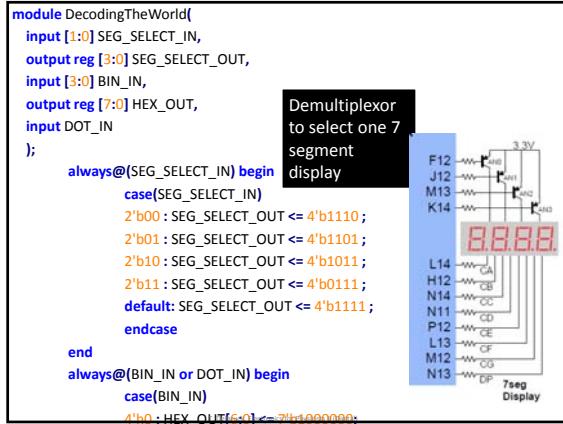

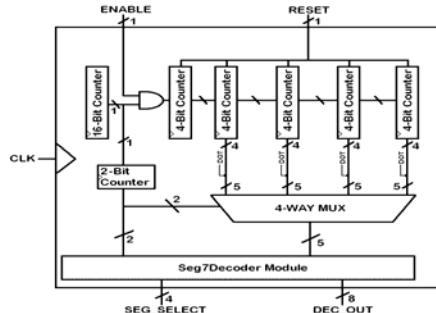
## 9. TimingTheWorldInDecimal

A decimal up timer that displays its result in seconds on the 7-segment display block



## 9. TimingTheWorldInDecimal

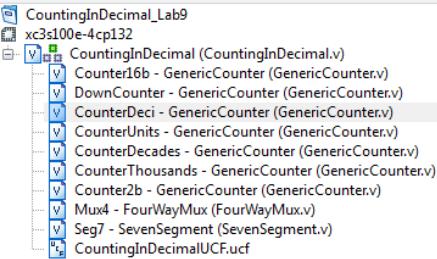

```
module GenericCounter(CLK, RESET, ENABLE_IN, TRIG_OUT, COUNT);
parameter COUNTER_WIDTH = 4;
parameter COUNTER_MAX = 9;

input CLK;
input RESET;
input ENABLE_IN;
output TRIG_OUT;
output [COUNTER_WIDTH-1:0] COUNT;

reg [COUNTER_WIDTH-1 : 0] Counter;
reg TriggerOut;

always@(posedge CLK)
begin
    if(RESET)
        Counter <= 0;
    else begin
        if(ENABLE_IN)
            if(Counter == COUNTER_MAX)
                Counter <= 0;
        else
            Counter <= Counter + 1;
    end
end
assign COUNT = Counter;
assign TRIG_OUT = TriggerOut;
endmodule
```

T. Delbrück, Electronics for Physicists II (Digital)

### GenericCounter

```
always@(posedge CLK) begin
    if(RESET)
        Counter <= 0;
    else begin
        if(ENABLE_IN) begin
            if(Counter == COUNTER_MAX)
                Counter <= 0;
            else
                Counter <= Counter + 1;
        end
    end
end
always@(posedge CLK) begin
    if(RESET)
        TriggerOut <= 0;
    else begin
        if(ENABLE_IN && Counter == COUNTER_MAX)
            TriggerOut <= 1;
        else
            TriggerOut <= 0;
    end
end
assign COUNT = Counter;
assign TRIG_OUT = TriggerOut;
endmodule
```

T. Delbrück, Electronics for Physicists II (Digital)

### GenericCounter

**[Module Type] [Unique Module Name] [...[Interface List]...];**

```
161 //Instantiate the 7 Segment Decoder
162     Seg7Decoder Seg7 (.SEG_SELECT_IN(StrobeCount),
163     .BIN_IN(MuxOut[3:0]),
164     .DOT_IN(MuxOut[4]),
165     .SEG_SELECT_OUT(SEG_SELECT),
166     .HEX_OUT(DEC_OUT)
167 );
```

**[Module Type] #(...[Parameter Definition List]...) [Unique Module Name] [...[Interface List]...];**

```
54 //The 16 bit Counter
55 GenericCounter #( .COUNTER_WIDTH(16),
56     .COUNTER_MAX(49999)
57 )
58 Bit16 (
59     .CLK(CLK),
60     .RESET(1'b0),
61     .ENABLE_IN(1'b1),
62     .TRIGG_OUT(Bit16TrigOut),
63     .COUNT(Bit16Count)
64 );
```

T. Delbrück, Electronics for Physicists II (Digital)

### Generic Instantiation

```
'timescale 1ns / 1ps
module CountingInDecimal(
    input CLK,
    input RESET,
    input ENABLE,
    output [3:0] SEG_SELECT,
    output [7:0] DEC_OUT
);

wire TriggerOut_16b, DownCounterEnable, TriggerOut_DownCounter, TriggerOut_CounterDeci,
TriggerOut_CounterUnits, TriggerOut_CounterDecades, TriggerOut_CounterThousands;
wire [3:0] DownCount;
wire [3:0] CountDeci;
wire [3:0] CountUnits;
wire [3:0] CountDecades;
wire [3:0] CountThousands;
wire [1:0] Select;
wire [1:0] Bin_Dec;
wire [1:0] DownCounterOut;
wire [1:0] CountDeciOut;
wire [1:0] CountUnitsOut;
wire [1:0] CountDecadesOut;
wire [1:0] CountThousandsOut;
```

T. Delbrück, Electronics for Physicists II (Digital)

```

wire TriggerOut_16b, DownCounterEnable, TriggerOut_DownCounter, TriggerOut_CounterDeci,
TriggerOut_CounterUnits, TriggerOut_CounterDecades, TriggerOut_CounterThousands;
wire [3:0] DownCount;
wire [3:0] CountDeci;
wire [3:0] CountUnits;
wire [3:0] CountDecades;
wire [3:0] CountThousands;
wire [1:0] Select;
wire [4:0] Bin_Dec;
wire [4:0] DownCounterOut;
wire [4:0] CountDeciOut;
wire [4:0] CountUnitsOut;
wire [4:0] CountDecadesOut;
wire [4:0] CountThousandsOut;

GenericCounter #(COUNTER_WIDTH(16), COUNTER_MAX(49999))
Counter16b(
    .CLK(CLK),
    .RESET(1'b0),
    .ENABLE_IN(1'b1),
    .TRIG_OUT(TriggerOut_16b)
);
assign DownCounterEnable = ENABLE && TriggerOut_16b [Digital]

GenericCounter #(COUNTER_WIDTH(16), COUNTER_MAX(49999))
CounterDeci(
    .CLK(CLK),
    .RESET(1'b0),
    .ENABLE_IN(1'b1),
    .TRIG_OUT(TriggerOut_CounterDeci)
);

```

```

GenericCounter #(COUNTER_WIDTH(16), COUNTER_MAX(49999))
Counter16b(
    .CLK(CLK),
    .RESET(1'b0),
    .ENABLE_IN(1'b1),
    .TRIG_OUT(TriggerOut_16b)
);

assign DownCounterEnable = ENABLE && TriggerOut_16b;

GenericCounter #(COUNTER_WIDTH(7), COUNTER_MAX(99))
DownCounter(
    .CLK(CLK),
    .RESET(RESET),
    .ENABLE_IN(DownCounterEnable),
    .TRIG_OUT(TriggerOut_DownCounter),
    .COUNT(DownCount)
);

GenericCounter #(COUNTER_WIDTH(4), COUNTER_MAX(9))
CounterDeci(
    .CLK(CLK),
    .RESET(RESET),
    .ENABLE_IN(TriggerOut_DownCounter),
    .TRIG_OUT(TriggerOut_CounterDeci) [Digital]
);

```

```

GenericCounter #(COUNTER_WIDTH(4), COUNTER_MAX(9))
CounterDeci(
    .CLK(CLK),
    .RESET(RESET),
    .ENABLE_IN(TriggerOut_DownCounter),
    .TRIG_OUT(TriggerOut_CounterDeci),
    .COUNT(CountDeci)
);

GenericCounter #(COUNTER_WIDTH(4), COUNTER_MAX(9))
CounterUnits(
    .CLK(CLK),
    .RESET(RESET),
    .ENABLE_IN(TriggerOut_CounterDeci),
    .TRIG_OUT(TriggerOut_CounterUnits),
    .COUNT(CountUnits)
);

GenericCounter #(COUNTER_WIDTH(4), COUNTER_MAX(5))
CounterDecades(
    .CLK(CLK),
    .RESET(RESET),
    .ENABLE_IN(TriggerOut_CounterUnits),
    .TRIG_OUT(TriggerOut_CounterDecades) [Digital]
);

```



```

assign CountDeciOut = {1'b0,CountDeci};
assign CountUnitsOut = {1'b1,CountUnits};
assign CountDecadesOut = {1'b0,CountDecades};
assign CountThousandsOut = {1'b0,CountThousands};

FourWayMux Mux4(
    .CounterDeci(CountDeciOut),
    .CounterUnit(CountUnitsOut),
    .CounterDec(CountDecadesOut),
    .CounterThousand(CountThousandsOut),
    .Select>Select,
    .Bin_Out(Bin_Dec)
);

SevenSegment Seg7(
    .SEG_SELECT_IN>Select,
    .SEG_SELECT_OUT(SEG_SELECT),
    .BIN_IN(Bin_Dec[3:0]),
    .HEX_OUT(DEC_OUT),
    .DOT_IN(Bin_Dec[4])
);
endmodule


```

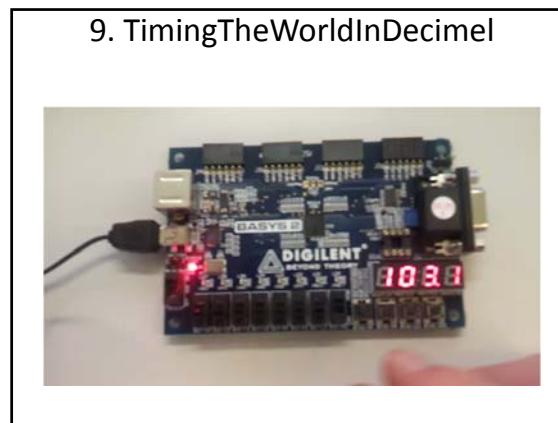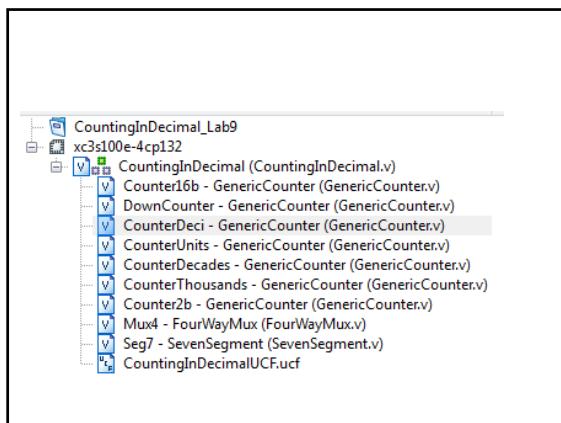


## "Gateway" lab exercises

10. [ColourTheWorld](#) - parameters in generics; VGA display control to generate sync signals and RGB colors ([see BASYS2 manual](#)).
11. [WorldOfStateMachines](#) - making **state machines** using sequential and combinational blocks (switch/case statements) and using ROM modules ([\\$readmemb](#)).
12. [WorldOfLinkedStateMachines](#) - multiple state machines linked by a master state machine.
13. [Snake](#) - a complete snake game.


## 10. ColorTheWorld

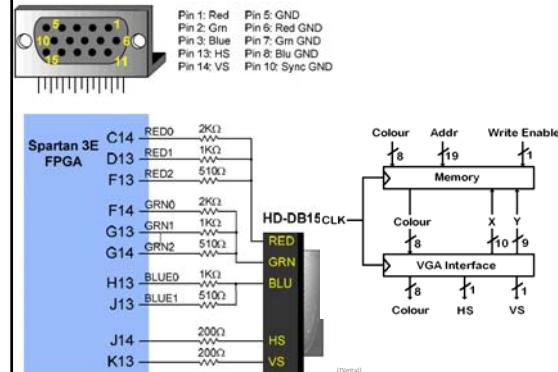

## VGA Control Signals

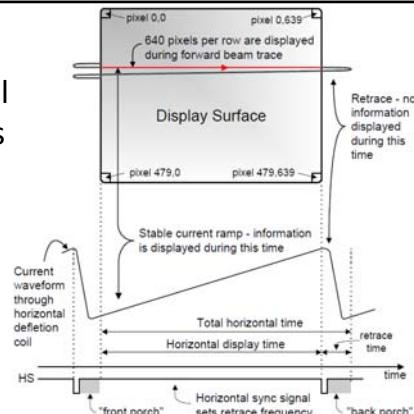



## 10. ColorTheWorld sync signals

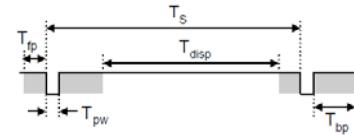


Symbol	Parameter	Vertical Sync			Horiz. Sync	
		Time	Clocks	Lines	Time	Clocks
$T_S$	Sync pulse	16.7ms	416,800	521	32 us	800
$T_{disp}$	Display time	15.36ms	384,000	480	25.6 us	640
$T_{pw}$	Pulse width	64 us	1,800	2	3.84 us	96
$T_{fp}$	Front porch	320 us	8,000	10	640 ns	16
$T_{bp}$	Back porch	928 us	23,200	29	1.92 us	48

T. Delbrück, Electronics for Physicists II (Digital)

## 10. ColorTheWorld sync signals

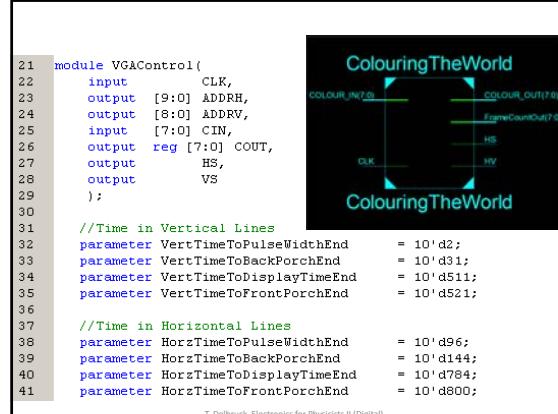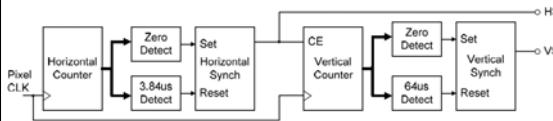

### 10. Wrapper module

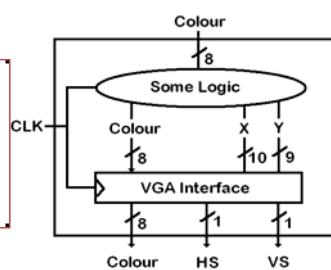

T. Döhring, Electronics for Physicists II (Digital)

### “Gateway” lab exercises

10. [ColourTheWorld](#) - parameters in generics; VGA display control to generate sync signals and RGB colors ([see BASYS2 manual](#)).
11. [WorldOfStateMachines](#) - making **state machines** using sequential and combinational blocks (switch/case statements) and using ROM modules ([\\$readmemb](#)).
12. [WorldOfLinkedStateMachines](#) - multiple state machines linked by a master state machine.
13. [Snake](#) - a complete snake game.

T. Döhring, Electronics for Physicists II (Digital)

### 11. WorldOfStateMachines

T. Döhring, Electronics for Physicists II (Digital)

### 11. WorldOfStateMachines

T. Döhring, Electronics for Physicists II (Digital)

### 11. WorldOfStateMachines

T. Döhring

### 11. WorldOfStateMachines

T. Döhring, Electronics for Physicists II (Digital)

### “Gateway” lab exercises

10. [ColourTheWorld](#) - *parameters* in generics; VGA display control to generate sync signals and RGB colors ([see BASYS2 manual](#)).
11. [WorldOfStateMachines](#) - making **state machines** using sequential and combinational blocks (switch/case statements) and using ROM modules (\$readmemb).
12. [WorldOfLinkedStateMachines](#) - multiple state machines linked by a master state machine.
13. [Snake](#) - a complete snake game.

### 12. WorldOfLinkedStateMachines

### 12. WorldOfLinkedStateMachines

### 12. WorldOfLinkedStateMachines

### 12. WorldOfLinkedStateMachines

### “Gateway” lab exercises

10. [ColourTheWorld](#) - *parameters* in generics; VGA display control to generate sync signals and RGB colors ([see BASYS2 manual](#)).
11. [WorldOfStateMachines](#) - making **state machines** using sequential and combinational blocks (switch/case statements) and using ROM modules (\$readmemb).
12. [WorldOfLinkedStateMachines](#) - multiple state machines linked by a master state machine.
13. [Snake](#) - a complete snake game.

12. Snake game

12. Snake game

12. Snake game